

Bill of Materials

TI DESIGNS

50mA Wireless Charger Booster Pack

TIDA-00881

Designator	Description	Manufacturer	PartNumber	Quantity
PCB1	Printed Circuit Board Main PCB	Any	TIDA-00668	1
PCB2	Printed Circuit Board PCB Coil	Any	TIDA-00668_C02	1
BT1	Battery Holder, CR2032, Retainer clip, TH	Memory Protection Devices	BS-7	1
C1, C13, C15	CAP, CERM, 4700 pF, 50 V, +/- 10%, X8R, 0402	TDK	C1005X8R1H472K	3
C2, C19	CAP, CERM, 0.47 µF, 25 V, +/- 10%, X7R, 0603	MuRata	GRM188R71E474KA12D	2
C3, C14, C16, C21, C23, C26, C27, C29	CAP, CERM, 0.1µF, 10V, +/-10%, X7R, 0402	MuRata	GRM155R71A104KA01D	8
C4, C5	CAP, CERM, 4.7 µF, 10 V, +/- 10%, X5R, 0402	TDK	C1005X5R1A475K050BC	2
C6, C9, C10, C20, C28	CAP, CERM, 0.01 µF, 50 V, +/- 5%, X7R, 0402	Kemet	C0402C103J5RACTU	5
C7	CAP, CERM, 0.022 µF, 16 V, +/- 10%, X7R, 0402	TDK	C1005X7R1C223K	1
C8	CAP, CERM, 4.7 µF, 16 V, +/- 10%, X5R, 0603	MuRata	GRM188R61C475KAAJ	1
C11, C12	CAP, CERM, 220 pF, 50 V, +/- 5%, C0G/NP0, 0402	MuRata	GRM1555C1H221JA01D	2
C17, C18, C22, C24, C25	CAP, CERM, 10 µF, 6.3 V, +/- 20%, X5R, 0603	Kemet	C0603C106M9PACTU	5
D1	LED, Green, SMD	Lite-On	LTST-C190GKT	1
Ferrite 1	Ferrite shield WE-FSFS	Würth	354005	1
FID1, FID2, FID3	Fiducial mark. There is nothing to buy or mount.	N/A	N/A	3
H1, H2, H3, H4, H5, H6, H7, H8	Machine Screw, Round, #4-40 x 1/4, Nylon, Philips panhead	B&F Fastener Supply	NY PMS 440 0025 PH	8
HS5, HS6, HS7, HS8	Standoff, Hex, 0.375"L #4-40 Nylon	Keystone	1902B	4
J1, J2, J3, J4, J5, J6, J7	Header, 100mil, 2x1, Gold, TH	Sullins Connector Solutions	PBC02SAAN	7
J8	Header (shrouded), 2mm, 2x1, R/A, SMT	JST Manufacturing	S2B-PH-SM4-TB(LF)(SN)	1
JP1, JP2	Header, 100mil, 10x2, Tin, SMT	Samtec	TSM-110-01-T-DV-P	2
L1	Inductor, Shielded, Ferrite, 4.7 µH, 1.2 A, 0.14 ohm, SMD	Coilcraft	EPL3015-472MLB	1
L2	Inductor, Wirewound, Ferrite, 10 µH, 0.47 A, 0.435 ohm, SMD	Würth Elektronik eiSos	74404024100	1
L3	Inductor, Wirewound, Ferrite, Wireless receiver coil 19mm Round	Würth Elektronik	760308101214	1
Q1	MOSFET, N-CH, 20 V, 6.7 A, SMD, 2.0x2.0, Height 0.8mm	Texas Instruments	CSD85301Q2	1
R1, R6	RES, 10.0 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW040210K0FKED	2
R2	RES, 5.36 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW04025K36FKED	1
R3	RES, 4.87 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW04024K87FKED	1
R4	RES, 1.30 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW04021K30FKED	1
R5	RES, 20.0 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW040220K0FKED	1
R7	RES, 1.50 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW04021K50FKED	1
R8, R10, R17, R23, R24	RES, 1.00 M, 1%, 0.063 W, 0402	Vishay-Dale	CRCW04021M00FKED	5
R9	RES, 196, 1%, 0.063 W, 0402	Vishay-Dale	CRCW0402196RFKED	1
R11	RES, 110 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW0402110KFKED	1
R12	RES, 8.06 M, 1%, 0.063 W, 0402	Vishay-Dale	CRCW04028M06FKED	1
R13, R21	RES, 0, 5%, 0.063 W, 0402	Vishay-Dale	CRCW04020000Z0ED	2

Designator	Description	Manufacturer	PartNumber	Quantity
R14	RES, 140 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW0402140KFKED	1
R16	RES, 4.53 M, 1%, 0.063 W, 0402	Vishay-Dale	CRCW04024M53FKED	1
R18	RES, 221, 1%, 0.063 W, 0402	Vishay-Dale	CRCW0402221RFKED	1
R19	RES, 2.21 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW04022K21FKED	1
R20	RES, 0.82, 1%, 0.125 W, 0402	Panasonic	ERJ-2BQFR82X	1
R22	RES, 2.7 k, 5%, 0.063 W, 0402	Vishay-Dale	CRCW04022K70JNED	1
SH-J1, SH-J4, SH-J5, SH-J6, SH-J7	Shunt, 100mil, Gold plated, Black	3M	969102-0000-DA	5
U1	Highly Integrated Wireless Receiver Qi (WPC v1.1) Compliant Power Supply, YFP0028APAL	Texas Instruments	BQ51003YFPR	1
U2	400 mA Single-Input, Single Cell Li-Ion Battery Chargers, YFP0006AFV	Texas Instruments	BQ25100YFP	1
U3	LOW INPUT VOLTAGE STEP-UP CONVERTER IN 6 PIN SC-70 PACKAGE, DCK0006A	Texas Instruments	TPS61220DCK	1
U4	Programmable Output Voltage Ultra-Low Power Buck Converter With Up to 50 mA Output Current, RGY0014A	Texas Instruments	TPS62736RGYR	1
U5	Cost-Effective Voltage and Current Protection Integrated Circuit for Single-Cell Li-Ion/Li-Polymer Batteries, DSE0006A	Texas Instruments	BQ29707DSER	1

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.